



相对简单CPU

物联1601 201608010424 潘婷婷

PS：因为课堂时间不够，没有能够在课堂上进行汇报，我把自己想表达的大致内容用蓝色字体写在PPT上了。

定义端口

地址引脚A[15..0]
数据引脚D[7..0]

```
entity rscpu is
    port (
        clk: in std_logic;
        reset: in std_logic;
        addrbus: out std_logic_vector(15 downto 0);
        databus: inout std_logic_vector(7 downto 0);
        readl: out std_logic;
        writel: out std_logic
    );
end entity;
```

寄存器

- ◆ 8位累加器AC
- ◆ 寄存器R
- ◆ 零标志位Z
- ◆ 16位的地址寄存器AR
- ◆ 16位的程序计数器PC
- ◆ 8位的数据寄存器DR
- ◆ 8位的指令寄存器IR
- ◆ 8位的临时寄存器TR

```
signal pc: std_logic_vector(15 downto 0);  
signal ac: std_logic_vector(7 downto 0);  
signal r: std_logic_vector(7 downto 0);  
signal ar: std_logic_vector(15 downto 0);  
signal ir: std_logic_vector(7 downto 0);  
signal dr: std_logic_vector(7 downto 0);  
signal tr: std_logic_vector(7 downto 0);  
signal z: std_logic;
```


状态操作码

```
constant fetch1: std_logic_vector(5 downto 0) := "000000";
constant fetch2: std_logic_vector(5 downto 0) := "000001";
constant fetch3: std_logic_vector(5 downto 0) := "000010";
constant fetch4: std_logic_vector(5 downto 0) := "000011";

constant nop1: std_logic_vector(5 downto 0) := "000100";

constant ldac1: std_logic_vector(5 downto 0) := "000101";
constant ldac2: std_logic_vector(5 downto 0) := "000110";
constant ldac3: std_logic_vector(5 downto 0) := "000111";
constant ldac4: std_logic_vector(5 downto 0) := "001000";
constant ldac5: std_logic_vector(5 downto 0) := "001001";

constant stac1: std_logic_vector(5 downto 0) := "001010";
constant stac2: std_logic_vector(5 downto 0) := "001011";
constant stac3: std_logic_vector(5 downto 0) := "001100";
constant stac4: std_logic_vector(5 downto 0) := "001101";
constant stac5: std_logic_vector(5 downto 0) := "001110";

constant mvac1: std_logic_vector(5 downto 0) := "001111";

constant movr1: std_logic_vector(5 downto 0) := "010000";
```

```
constant jump1: std_logic_vector(5 downto 0) := "010001";
constant jump2: std_logic_vector(5 downto 0) := "010010";
constant jump3: std_logic_vector(5 downto 0) := "010011";

constant jmpzn1: std_logic_vector(5 downto 0) := "010100";
constant jmpzn2: std_logic_vector(5 downto 0) := "010101";

constant jpnzn1: std_logic_vector(5 downto 0) := "010110";
constant jpnzn2: std_logic_vector(5 downto 0) := "010111";

constant jmpzy1: std_logic_vector(5 downto 0) := "011000";
constant jmpzy2: std_logic_vector(5 downto 0) := "011001";
constant jmpzy3: std_logic_vector(5 downto 0) := "011010";

constant jpnzy1: std_logic_vector(5 downto 0) := "011011";
constant jpnzy2: std_logic_vector(5 downto 0) := "011100";
constant jpnzy3: std_logic_vector(5 downto 0) := "011101";

constant add1: std_logic_vector(5 downto 0) := "011110";
constant sub1: std_logic_vector(5 downto 0) := "011111";
constant ina1: std_logic_vector(5 downto 0) := "100000";
constant cla1: std_logic_vector(5 downto 0) := "100001";
constant and1: std_logic_vector(5 downto 0) := "100010";
constant or1: std_logic_vector(5 downto 0) := "100011";
constant xor1: std_logic_vector(5 downto 0) := "100100";
constant not1: std_logic_vector(5 downto 0) := "100101";
```


取指令和译码

FETCH1: $AR \leftarrow PC$
FETCH2: $DR \leftarrow M, PC \leftarrow PC + 1$
FETCH3: $IR \leftarrow DR$
FETCH4: $AR \leftarrow PC$

根据每个状态需要完成的操作
产生相应的控制信号。

```
case state is
  when fetch1 =>      --AR-PC|
    arload <= '1';
    arinc  <= '0';
    pload  <= '0';
    pcinc  <= '0';
    drload <= '0';
    trload <= '0';
    irload <= '0';
    rload  <= '0';
    aload  <= '0';
    acinc  <= '0';
    writel <= '0';
    readl  <= '0';
    membus <= '0';
    pcbus  <= '1';
    drbus  <= '0';
    trbus  <= '0';
    rbus   <= '0';
    acbus  <= '0';
    cle    <= '0';
    busmem <= '0';
```

数据通路

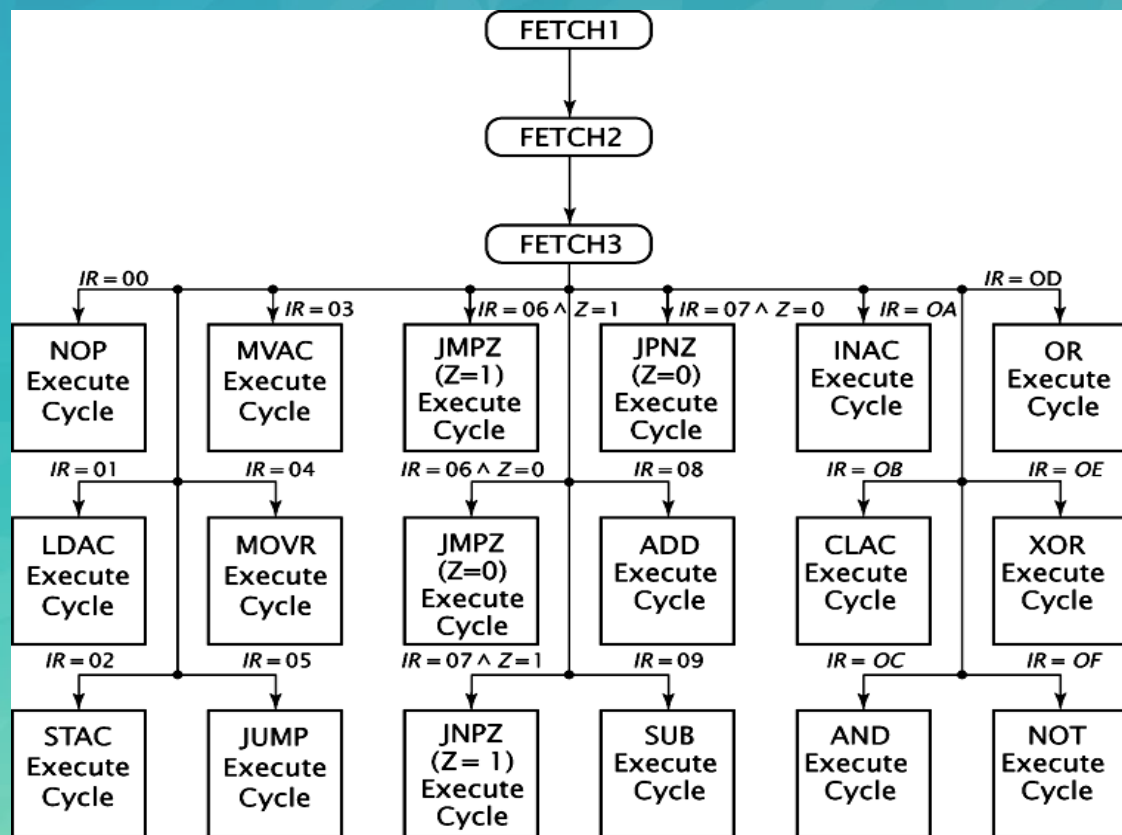

译码。从FETCH4状态到各指令
执行状态序列的第一个状态。

```
case state is
    when fetch1 =>
        nextstate <= fetch2;
    when fetch2 =>
        nextstate <= fetch3;
    when fetch3 =>
        nextstate <= fetch4;
    when fetch4 =>
        case ir is
            when RSNOP =>
                nextstate <= nop1;
            when RSCLAC =>
                nextstate <= clac1;
            when RSSTAC=>
                nextstate <= stac1;
            when RSLDAC=>
                nextstate <= ldac1;
            when RSINAC=>
                nextstate <= inac1;
            when RSMVAC=>
                nextstate <= mvac1;
            when RSADD=>
                nextstate <= add1;
            when RSSUB=>
                nextstate <= sub1;
```


数据通路

```
-- address and data bus
addrbus <= ar;
databus <= dr when busmem='1' else "ZZZZZZZZ";
```

```
--the bus
thebus<=pc
    "00000000"&databus
    "00000000"&r
    "00000000"&ac
    dr&tr
    "00000000"&dr
    "ZZZZZZZZZZZZZZZZZZ";
    when pcbus='1'
    when membus='1'
    when rbus='1'
    when acbus='1'
    when (trbus='1' and drbus='1')
    when (drbus='1' and trbus/='1')
    else
    else
    else
    else
    else
    else
```

```
alu_result <= std_logic_vector(unsigned(ac)-unsigned(thebus(7 downto 0))) when state=subl else
std_logic_vector(unsigned(ac)+unsigned(thebus(7 downto 0))) when state=addl else
std_logic_vector(ac and thebus(7 downto 0)) when state=andl else
std_logic_vector(ac or thebus(7 downto 0)) when state=orl else
std_logic_vector(ac xor thebus(7 downto 0)) when state=xorl else
std_logic_vector( not ac) when state=notl else
thebus(7 downto 0);
```

根据控制信号执行相应的操作

数据通路

DR和TR必须被同时送到总线上，DR在位15..8，TR在位7..0。

```
dr&tr          when (trbus='1' and drbus='1')      else  
"00000000"&dr  when (drbus='1' and trbus/='1')      else  
"0000000000000000"
```


数据通路

零标志位Z：每次执行算术运算或者逻辑运算的时候，它都将被置位。

```
if(state=ADD1 or state=SUB1 or state=NOT1 or state=AND1 or state=OR1 or state=XOR1) then
if(alu_result="00000000") then
    z<='1';
else
    z<='0';
end if;
end if;
```

```
if(acinc='1') then
    ac <= std_logic_vector(unsigned(ac)+1);
    if(ac="11111111") then z<='1';
    else z<='0';
    end if;
end if;
```

数据通路

```
if(rising_edge(clk)) then
  --pc
  if(reset='1') then
    pc <= X"0000";
    state <= fetch1;
  else
    --pc <= nextpc;
    state <= nextstate;
  end if;

  if(arload='1') then
    ar <= thebus;
  end if;
  if(pcload='1') then
    pc <= thebus;
  end if;
  if(drload='1') then
    dr <= thebus(7 downto 0);
  end if;
  if(trload='1') then
    tr <= dr;
  end if;
  if(irload='1') then
    ir <= dr;
  end if;
  if(rload='1') then
    r <= thebus(7 downto 0);
  end if;
```


建立一条从DR输出端到IR输入端的直接通路，使得 $IR \leftarrow DR$ 不使用内部总线。👉

```
if(trload='1') then
  tr <= dr;
end if;
```

TR只从DR接受数据，所以CPU可以包含一条从DR的输出到TR的输入的直接通路。👉


```
if(irload='1') then
  ir <= dr;
```

数据通路

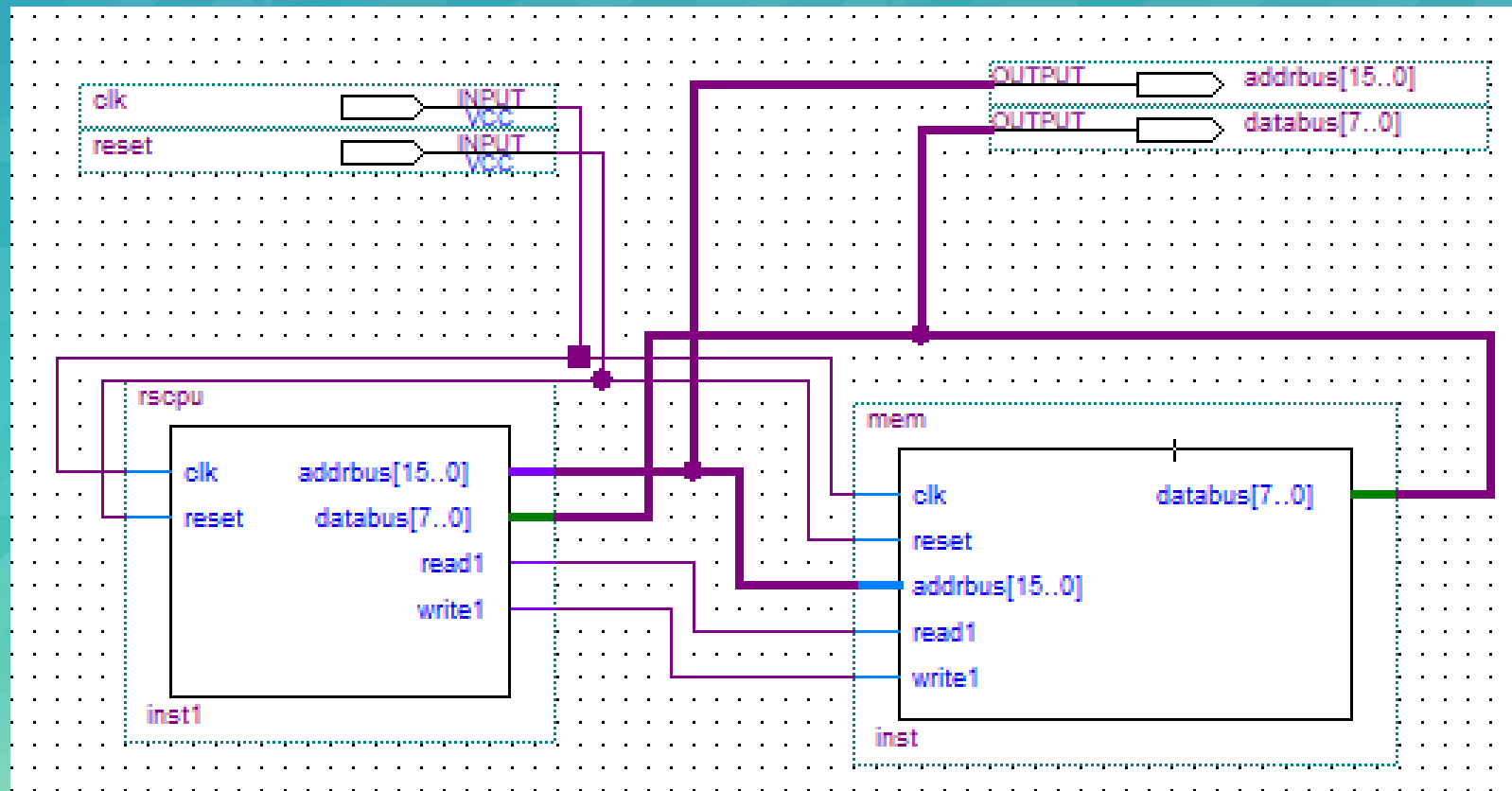


根据同学的建议，不使用VHDL程序，而采用模块图连接的方式将cpu和mem连接起来。

仿真结果

 

```
constant total_addr : integer := 29;  
constant i_addr : integer := 30;  
constant n_addr : integer := 31;  
constant loop_addr : integer := 7;
```

```
signal memdata: memtype(4095| downto 0) := (  
0 => RSCLAC,  
1 => RSSTAC,  
2 => std_logic_vector(to_unsigned(total_addr, 8)),  
3 => X"00",  
4 => RSSTAC,  
5 => std_logic_vector(to_unsigned(i_addr, 8)),  
6 => X"00",  
7 => RSLDAC, -- loop  
8 => std_logic_vector(to_unsigned(i_addr, 8)),  
9 => X"00",  
10 => RSINAC,  
11 => RSSTAC,  
12 => std_logic_vector(to_unsigned(i_addr, 8)),  
13 => X"00",  
14 => RSMVAC,  
15 => RSLDAC,  
16 => std_logic_vector(to_unsigned(total_addr, 8)),  
17 => X"00",  
18 => RSADD,
```

 

```

gen_controls: process(state)
begin
    pcbus <= fetch1 or fetch3;
    trbus <= LDAC3 or STAC3 or JUMP3 or JMPZY3 or JPNZY3;
    rbus  <= MOVR1 or ADD1 or SUB1 or AND1 or OR1 or XOR1;
    acbus <= STAC4 or MVAC1;
    drbus <= fetch3 or ldac2 or ldac5 or stac3 or stac5 or jump3 or jmpzy3 or jpnzy3;
    membus<= FETCH2 or LDAC1 or LDAC2 or LDAC4 or STAC1 or STAC2 or JUMP1 or JUMP2 or JMPZY1 or JMPZY2 or JPNZY1 or JPNZ
    busmem<= STAC5;

    cle  <= clac1;
    pcinc <= fetch2 or ldac1 or ldac2 or stac1 or stac2 or jmpzn1 or jmpzn2 or jpnzn1 or jpnzn2;
    arinc <= LDAC1 or STAC1 or JUMP1 or JMPZY1 or JPNZY1;

    arload<= FETCH1 or FETCH3 or LDAC3 or STAC3;
    pcload<= jump3 or jmpzy3 or jpnzy3;
    drload<= fetch2 or ldac1 or ldac2 or ldac4 or stac1 or stac2 or stac4;

```

老师写的代码是按不同的状态产生相应的控制信号，但是写代码的时候感觉有点繁琐，因此打算用这样的方式来写，后来又想到这样写每个状态都得赋值为1位的数，或者创建新的变量，所以就放弃了。

②

状态	功能	状态	功能
FETCH1	T0	JMPZY1	IJMPZ \wedge Z \wedge T3
FETCH2	T1	JMPZY2	IJMPZ \wedge Z \wedge T4
FETCH3	T2	JMPZY3	IJMPZ \wedge Z \wedge T5
NOP1	INOP \wedge T3	JMPZN1	IJMPZ \wedge Z' \wedge T3
LDAC1	ILDAC \wedge T3	JMPZN2	IJMPZ \wedge Z' \wedge T4
LDAC2	ILDAC \wedge T4	JPNZY1	IJPNZ \wedge Z' \wedge T3
LDAC3	ILDAC \wedge T5	JPNZY2	IJPNZ \wedge Z' \wedge T4
LDAC4	ILDAC \wedge T6	JPNZY3	IJPNZ \wedge Z' \wedge T5
LDAC5	ILDAC \wedge T7	JPNZN1	IJPNZ \wedge Z \wedge T3

FETCH3: IR \leftarrow DR, AR \leftarrow PC

```

case state is
  when fetch1 =>
    nextstate <= fetch2;
  when fetch2 =>
    nextstate <= fetch3;
  when fetch3 =>
    nextstate <= fetch4;
  when fetch4 =>
    case ir is
      when RSNOP =>
        nextstate <= nop1;
      when RSCLAC =>
        nextstate <= clac1;

```

上次报告CPU的时候，讨论了fetch3状态，因为fetch3时将数据加载到IR寄存器中，同时还要根据IR寄存器中的值判断下一状态，可能会有冲突，发生错误。后来我仔细看了PPT，我认为PPT是正确的，因为它有明确每个指令的执行时间，fetch是T2，而后面进行判断下一状态是T3。不过我们没有去实现让这两步操作隔一个时钟，因此我还是采用的fetch4的方法。



感谢您的观看与欣赏

Happy New Year!